

大同大學 九十 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. (a) For an abrupt PN junction the depletion-region width as a function of voltage is

given by
$$W = \left[\frac{2\epsilon_{si}}{q} \left(\frac{1}{N_A} + \frac{1}{N_D} \right) (V_0 - V) \right]^{\frac{1}{2}}$$
, where V_0 is the built-in voltage,

ϵ_{si} is the permittivity of Si. Derive the junction capacitance $c = \frac{c_0}{\sqrt{1-V/V_0}}$,

define the c_0 . (5%)

- (b) If $N_A = 10^{18} \text{ cm}^{-3}$, $N_D = 10^{15} \text{ cm}^{-3}$ and PN junction area $A = 6 \times 10^{-4} \text{ cm}^2$, calculate the junction capacitance for reverse-biased of 10 Volts. (the dielectric constant of Si :11.9, intrinsic carrier concentration of Si:






$n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$, permittivity of vacuum: $8.85 \times 10^{-14} \text{ F/cm}$,

$T = 27^\circ \text{C}$) (8%)

2. A logic gate has a delay-power product of 1 pJ . The gate power dissipation is 1 mW . What is the gate switching time? (4%)
3. For a CMOS gate shown in fig.p3, derive the transition points of

     - (a) $M_2: V_{out} = V_{in} - V_{tp}$ (b) $M_1: V_{out} = V_{in} - V_{tm}$ where V_m and

V_{tp} are the threshold voltage of NMOS and PMOS respectively. (12%)



4. Please write down the output function Y in terms of inputs in the logic circuit as shown in fig.p4. (5%)
5. The floating-gate transistor used as an EPROM cell shown in fig.p5, please sketch $i_D - v_{GS}$ curve. (6%)

<背面繼續>

大同大學 九十 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所


第 3 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

6. Sketch the timing waveforms; V_{o1} , V_{o2} and V_{I1} for the circuit shown in fig.p6. (12%)
7. Consider the circuit shown in fig.p7.
 - (a) Assuming the opamp is ideal, derive the transfer function $T(s)$. (12%)
 - (b) Determine the type of the filter. (3%)

8. Consider the cascode current mirror as shown in fig.p8 , where all the transistors are identical with $\mu_n C_{ox}=100\mu A/V^2$, $V_{tn}=0.8 V$ and $W/L=8$.

 - (a) What is the maximum resistance R for the cascode current mirror shown in the figure without any transistors entering the triode region? (Neglect the body effect and the channel length modulation effect of the transistors.) (5%)
- (b) Estimate the output resistance seen into transistors $M3$, where $\lambda=0.025 V^{-1}$. (5%)



9. For the circuit shown in fig.p9 , the parameters for the NPN transistor are $V_{BE(on)}=0.7V$, $\beta=120$ and $V_A=100V$. The parameters for the NMOS transistor are $\mu_n C_{ox}=100\mu A/V^2$, $V_{tn}=0.8 V$ and $W/L=8$. ($V_T=25mV$)
 - (a) If the bias current of the NMOS transistor is set to be $100\mu A$, find the resistance for R_s . (Neglect the body effect and the channel length modulation effect of the NMOS transistor.) (5%)
 - (b) Calculate the small-signal midband gain $A_v=v_{o2}/v_i$. (5%)
 - (c) Estimate the upper 3-dB frequency (in Hz). (Neglect the internal capacitors of the transistors.) (3%)
 - (d) Determine the pole and zero introduced by C_{C1} . (5%)
 - (e) If a capacitor of $100pF$ is connected between v_{o1} and v_{o2} , estimate the upper 3-dB frequency again. (5%)

