

大同大學 九十一 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

- The ideal metal-oxide-semiconductor structure is shown in Fig. P1, the doping concentration (in $p-Si$)= N_A , the oxide thickness= x_o , the depletion width (in $p-Si$)= x_d , ϵ_s (permittivity of Si)= $11.7 \epsilon_0$ and ϵ_{ox} (permittivity of oxide)= $3.9 \epsilon_0$.
 - Derive the electric field $E(x)$ in the region $0 \leq x \leq x_d$ for the depletion case ($V_G > 0$).
 - Find an expression for electric field (E_{ox}) in the oxide in terms of N_A and x_d etc..
 - Sketch the $E(x)$ vs x plot over the region $-x_o \leq x \leq x_d$.

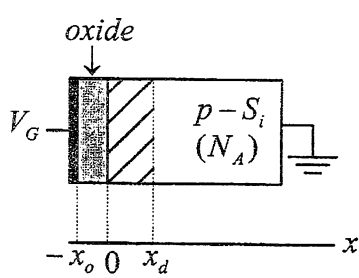


Fig. P1

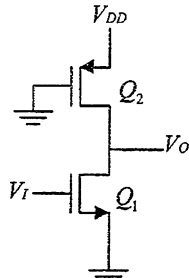


Fig. P2

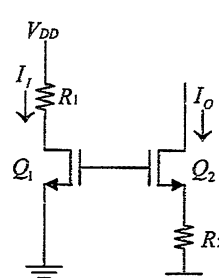


Fig. P3

- (10%) Refer to Fig. P2, $V_{DD} = 5V$, MOS threshold voltage $V_t = V_{tn} = -V_{tp} = 1V$, $K_r = \frac{K_n}{K_p} = 9$, where $K_{n,p} = (\mu C_{ox} W/L)_{n,p}$. The gate threshold voltage V_M is by definition the value of V_I for which $V_O = V_I$. (a) Derive V_M in terms of V_t , V_{DD} and K_r . (b) Calculate V_M .
- (10%) Refer to Fig. P3, both transistors operate in saturation region, $I_I = 0.1mA$, $R_2 = 4K\Omega$, $\mu_n C_{ox} \frac{W}{L} = 5mA/V^2$, and $V_{tn1} = V_{tn2}$. Neglect the body effect and channel length modulation, calculate I_O .
- (8%) Refer to Fig. P4 (a) and (b), derive the relationship between V_O and V_I , sketch V_O vs V_I plot.

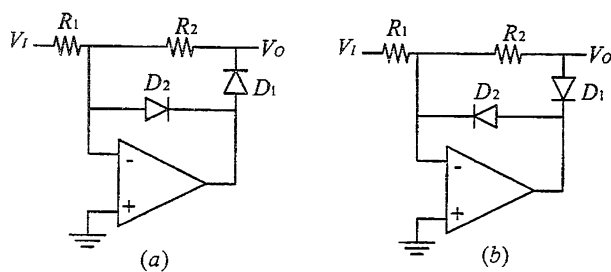


Fig. P4

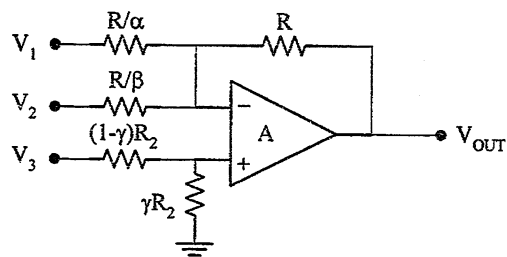


Fig. P5

- (8%) Consider the circuit shown in Fig. P5, where α, β and γ are constants and $0 \leq \gamma \leq 1$. If the gain of the opamp is finite and denoted by A , write the output function. (22%)
- (a) Consider the circuit shown in Fig. P6(a), estimate the midband gain and the upper $-3dB$ frequency. ($\mu_n C_{ox} (W/L) = 400 \mu A/V^2$, $V_{tn} = 0.7V$, $C_{gs} = 0.2pF$ and $C_{gd} = 50fF$)
 (b) The bias current I_B in the circuit shown in Fig. P6(b) is the same as that in Fig. P6(a). If the midband gain of the circuit in Fig. P6(a) is denoted by K , what is the low-frequency gain of the circuit shown in Fig. P6(b). Also estimate its upper $-3dB$ frequency.

< 轉 背 面 >

大同大學 九十一 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 3 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

〈接前頁〉

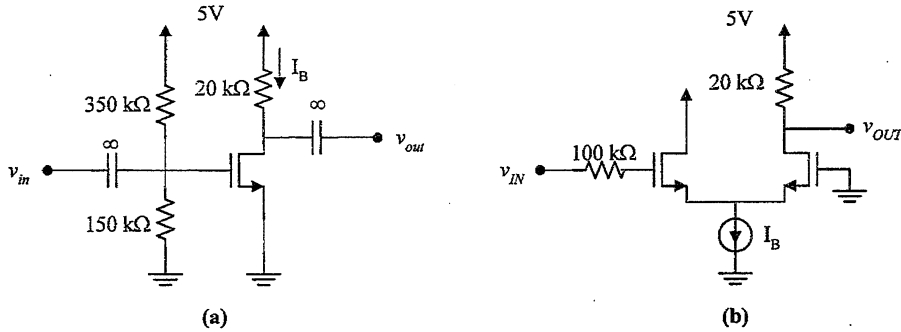


Fig.P6

7. (12%) Consider the circuit shown in Fig.P7, where $\mu_n C_{ox} = 2.5 \times \mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$, $V_{in} = -V_{tp} = 0.7\text{V}$, $(W/L)_1 = (W/L)_3 = (W/L)_4 = 8$, $(W/L)_2 = 32$, and $(W/L)_5 = (W/L)_6 = (W/L)_7 = 20$.
- (a) If all the transistor are operating in the saturation region with $I_{out} = 100 \mu\text{A}$, find the required resistance R_S . (Neglect the channel-length modulation and body effects.)
- (b) Estimate the output resistance (R_{out}) seen into the drain of transistor M4. ($\lambda = 0.025 \text{ V}^{-1}$)

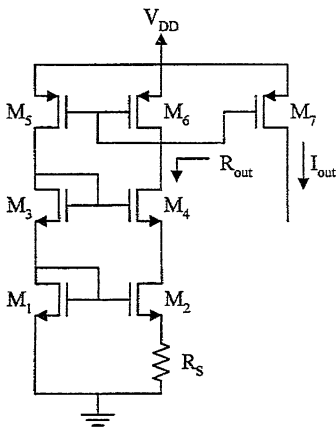


Fig.P7

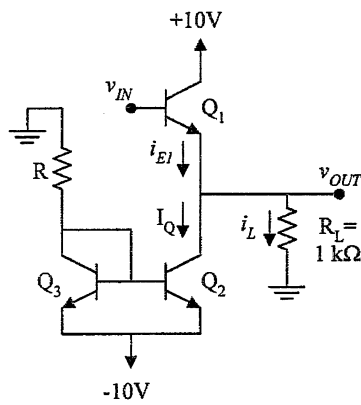


Fig.P8

8. (12%) A class-A emitter follower biased with a constant-current source is shown in Fig.P8, where the transistors parameters are $\beta = 100$, $V_{BE} = 0.7\text{V}$ and $V_{CE(sat)} = 0.2\text{V}$.
- (a) What is the maximum and minimum values for i_L ?
- (b) What is the minimum value for I_Q ? Determine the value of R to produce the corresponding current.

9. (8%) The open-loop gain of an amplifier is given by $A(s) = \frac{1000}{(1 + \frac{s}{\omega_b})^3}$. The amplifier is

placed in a negative-feedback loop with transfer function β , a real constant.

Find the maximum value of β for the amplifier to be stable.