

# 大同大學九十二學年度研究所碩士班入學考試試題

## 考試科目：電子學

所別：電機工程研究所

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. (8%)(a). As shown in Fig. p1, initially  $V_o(t=0) = 0$ , set  $V_{in} = V_{DD}$  at  $t=0$ , show that


$V_o(t) = V_f \left[ \frac{t/\tau}{1 + (t/\tau)} \right]$ , define  $V_f$  and  $\tau$  in terms of  $V_{DD}$ ,  $C$ ,  $V_t$ ,  $K_n$  ( $= \mu_n C_{OX} W/L$ ) etc..

- (b). What is the steady state output voltage  $V_f$  in terms of parameters above.

- 2. (6%)** Given nMOS threshold voltage  $V_t = V_{t0} + \frac{\sqrt{2q\epsilon_{Si}N_A}}{C_{ox}} (\sqrt{|2\phi_f| + V_{SB}} - \sqrt{|2\phi_f|})$ , derive

$g_{mb} = \chi g_m$ , where  $g_m$  and  $g_{mb}$  are the transconductance and body transconductance respectively, define the  $\chi$ .

3. (10%) For the ideal opamp circuit shown in Fig. p3 derive an expression for the transfer function  $V_o/V_i$ . Find expressions for the magnitude and phase of the response.

 

**Fig. p1**

 


Fig. p3

4. (20%) Consider the cascode gain stage of Fig. p4, where  $\mu_n C_{ox} = 2.5 \times \mu_p C_{ox} = 100 \mu\text{A/V}^2$ ,  $V_{tn} = -V_{tp} = 0.7\text{V}$ ,  $\lambda_n = \lambda_p = 0.025 \text{ V}^{-1}$ ,  $(W/L)_1 = (W/L)_2 = (W/L)_3 = (W/L)_4 = 50$ ,  $(W/L)_5 = (W/L)_6 = (W/L)_7 = (W/L)_8 = 20$  and  $(W/L)_9 = (W/L)_{10} = 100$ .

- (a). Find the value for  $R_B$ .
  - (b). Estimate the low-frequency differential voltage gain (in dB). (Neglect the body effect.)
  - (c). Estimate  $-3\text{dB}$  bandwidth and unity-gain bandwidth.
  - (d). Calculate the input common-mode range.


 


Fig. p4

 

**Fig. p5**

 


Fig.p6

5. (10%) For the circuit shown in Fig. p5, the opamp has an open-loop gain ( $A$ ) of  $10^4$  and output resistance  $r_o=1\text{k}\Omega$ .

- (a). Find the voltage gain ( $V_o/V_{in}$ ) and output resistance ( $R_{out}$ ) for the closed-loop circuit.

- (b). If the bandwidth of the opamp is 100 Hz, what is the bandwidth of the closed-loop circuit?

## 〈背面迷墳〉

# 大同大學九十二學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 2/2 頁

〈按前頁〉

註：本次考試 不可以參考自己的書籍及筆記；不可以使用字典；可以使用計算器。


6. (10%) Consider a class-B output as shown in Fig.p6 with a 1kHz sine-wave input of 2.5V peak.

(a). Assuming  $|V_{BE}|=0.7V$ , draw the waveforms for  $V_{in}$  and currents  $i_1$ ,  $i_2$  and  $i_L$ .

(b). Calculate the root-mean-square value for  $i_1$ .

7. (12%) (a) Determine the transistors operated in which region (linear, saturation, or cutoff region) with  $R_C = 1 K\Omega$ ,  $R_B = 4.3 K\Omega$ ,  $V_{CC} = V_{BB} = 5$  volts,  $\beta_F = 50$ ,  $V_{BE(on)} = 0.7$  volts and  $V_{CE(sat)} = 0$  volts,  $V_{SD} = 0.4$  volts.

 (b) Determine the output voltage of each circuit below.



8. (12%) An inverter drives an identical inverter with the propagation delay of

$t_{pInv} = t_{PHL} = t_{PLH}$ , assume the minimum size of transistors are  $(W/L)_P = 2, (W/L)_N = 2$ .

(a). Draw the conventional CMOS schematic diagram of the logic function

$F = \text{NOT}((A+B)\bar{C}+DE)$  with the minimum delay (consider the diffusion capacitance effect).

(b). If the sizes of all transistors are same as the inverter, find the propagation delay ( $t_{PHL}, t_{PLH}$ ) of this logic circuit in the worst case.

9. (12 %) Determine the logic function in the following circuits.

