

大同大學 九十三年年度研究所碩士班入學考試試題

考試科目：電力系統

所別：電機工程研究所

第 $\frac{1}{2}$ 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 不可以使用計算器。

1. A three-phase motor is used to drive a pump. It is observed that the motor speed decreased from 998 rpm at no load to 950 rpm at full load. (15%)

- Is this a synchronous or induction motor?
- Estimate the frequency of the applied voltage in Hz.
- How many poles does the motor have?

2. Explain the following items. (10%)

- Compensation-winding of DC machine.
- Slip and slip region of the induction machine (motor and generator).

3. A three-phase line has an impedance of $0.4 + j2.7 \Omega$ per phase. The line supplies two loads connected in parallel. The load 1 is 560.1 kVA at 0.707 power factor lagging. The load 2 is 132 kW at unity power factor. The line-to-line voltage at the load end is 3810.5 V. Determine

- the magnitude of the line voltage at the source end of the line,
- real and reactive power supplied at the sending end of the line. (10%)

4. A three-phase short circuit occurs at the generator bus (bus 1) for the system shown in Fig. 4. Neglecting pre-fault currents and assuming that the generator is operating at its rated voltage. (25%)

- Draw the equivalent reactance diagram with corresponding per-unit values are marked. Choose the base values of 25 MVA and 13.8 kV on the generator side.
- Calculate the subtransient fault current of per-unit value.

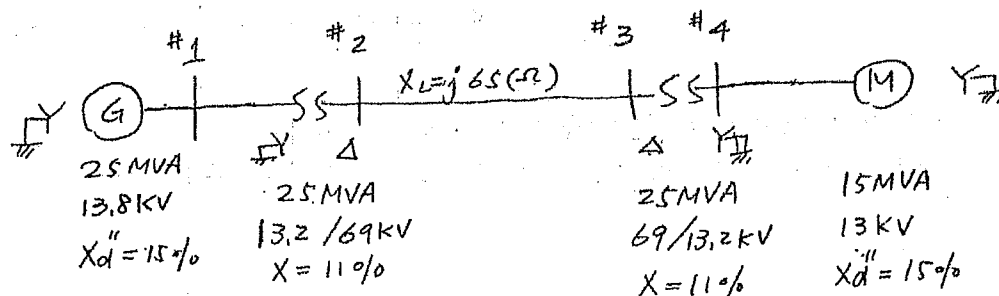


Fig. 4

5. An industrial dryer operates at 600 Volt and requires 50 A. The unit consists of a fan in parallel with a heater. The fan draws 20 kW and has a lagging power factor of 0.8. Use a power triangle to find the resistance of the heater, assuming that it has unity power factor. (15%)

<背面繼續>

大同大學 九十三年年度研究所碩士班入學考試試題

考試科目：電力系統

所別：電機工程研究所

第 2/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 不可以使用計算器。

<接前頁>

6. In Fig. 6, load 1 has a balanced delta (Δ) configuration, while load 2 has a balanced wye (Y) configuration, with the frequency of 60 Hz, $V_{ab} = 380$ V(rms), $Z_l = 3 + j\Omega$, $Z_{\Delta 1} = 24 + j12\Omega$, and $Z_{Y2} = 5 + j10\Omega$. (15%)
- Find the average power drawn by each load.
 - Find the power factor seen by the generator.
 - Find the capacitance C_{Δ} added in parallel to the load, increasing the power factor to 0.95 lagging.

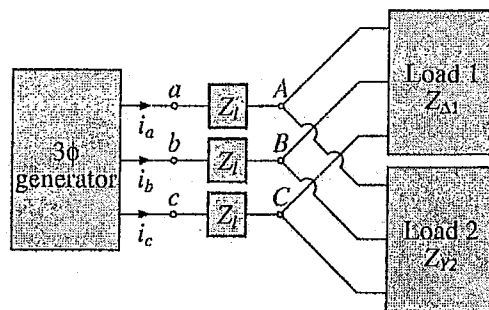


Fig. 6

7. Consider a three-wire composite system with two single-phase loads and two wattmeters, as shown in Fig. 7. The given values are $V_{ab} = 380\angle 0^\circ$ V(rms) and $Z_{\Delta} = 8\angle 60^\circ\Omega$ for the 3ϕ load (Δ configuration). (10%)
- Find I_a , I_b , and I_c .
 - Find the resultant readings of $P_1 + P_2$.

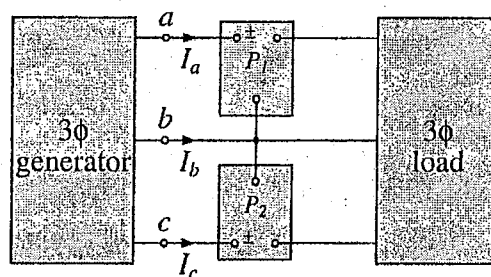


Fig. 7