

大同大學 九十四 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. (12%) In Fig. 1, $\mu C_{ox}(W/L) = 1mA/V^2$ for both NMOS and PMOS, $V_{tn} = -V_{tp} = 1V$ and neglect the body effect.

Calculate I_{Dn} , I_{Dp} and V_O when $V_i = 2.5V, -2.5V$.

 


Fig. 1

 


Fig. 2

2. (22%) Refer to Fig. 2, neglect the body effect, the channel modulation, and the Early effect. The parameters for BJT are $\beta = 100$ and $I_S = 10^{-14} A$, for PMOS, $\mu_p C_{ox} = 50 \mu A/V^2$, $W/L = 100$ and $V_{tp} = -0.7V$.
- (a) In case $v_{IN} = 0$, calculate the value of V_1 and V_2 which will keep $i_1 = i_2 = 100 \mu A$.
- (b) With V_1 and V_2 as calculated as in part (a), apply an ideal source v_{IN} , sketch the small signal equivalent circuit and calculate the input resistance R_i , output resistance R_o and small signal voltage gain.
3. (8%) For the feedback circuit shown in Fig.3, the amplifier has a low-frequency gain of 2000 and a single-pole rolloff at 1 kHz. If β is 0.5, find the low-frequency gain and the bandwidth of the feedback circuit.
4. (15%) Consider the differential pair shown in Fig. 4, where W/L values are given in the figure, $\mu_p C_{ox} = 25 \mu A/V^2$ and $V_{tp} = -0.6V$. Neglect the channel length modulation effect.
- (a) Find the minimum value of v_{id} that causes M1 to conduct the entire current I .
- (b) Find the equivalent small-signal transconductance for the differential pair (input: v_{id} , and output: $i_{D1} - i_{D2}$).
- (c) What is the lowest value of V_{CM} ($v_{id} = 0$) for which M1 and M2 remain in saturation?

 


Fig. 3

 


Fig. 4

<背面繼續>

大同大學 九十四 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 2/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

〈接前頁〉

5. (10%) Consider the common-source amplifier shown in Fig. 5, where W/L values are given in the figure, $\mu_n C_{ox} = 2.5 \times \mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$, $V_{tn} = -V_{tp} = 0.6\text{V}$, $\lambda_n = 0.04\text{V}^{-1}$ and $\lambda_p = 0.08\text{V}^{-1}$.
- (a) Estimate the low-frequency voltage gain, where V_{IN} is given such that all transistors are in the saturation region.
- (b) If $C_{gd1} = 5\text{fF}$ and $C_{gs1} = 80\text{fF}$, estimate the total capacitance seen by R_{IN} .

 


Fig. 5

 


Fig. 6

6. (18%) Determine the mode of operation (cutoff, active or saturated mode) for each transistor in the circuit shown in Fig. 6 when (a) $V_{in} = 0\text{V}$, (b) $V_{in} = 5\text{V}$. And assume $\beta_F = 100$, $\beta_R = 0.5$, $V_{BE(ON)} = 0.7\text{V}$, $V_{BE(sat)} = 0.8\text{V}$ and $V_{CE(sat)} = 0.1\text{V}$. Why? Describe it briefly.
7. (15%) (a) Draw a CMOS inverter with $V_{DD} = 5\text{V}$, where $\mu_n C_{ox} = 115 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 30 \mu\text{A}/\text{V}^2$, and $V_{tn} = |V_{tp}| = 1\text{V}$.
- (b) Assuming the $W/L = 1$ of the NMOS device, design the inverter with a 2.5V logic switching threshold voltage. What is the W/L of the PMOS device?
- (c) Draw the curve of current ($I_{DN} = |I_{DP}|$) vs V_{in} , as V_{in} from 0V to 5V. Label the important points, like the voltages of start point and end point of the current flow.
- (d) When the inverter with the load capacitor C_L , how does change the C_L affect the current curve in part (c)?