

大同大學 九十五 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. (12%) Consider the circuit of Fig. 1. For (a). $v_i = 1$ V and (b). $v_i = -1$ V, calculate the voltages at v_o and v_A . Assume that the op amp is ideal and its output saturates at ± 12 V, the diode has a 0.7 V drop at 1 mA current, and its voltage drop changes by 0.1 V per decade of current change.
2. (12%) Refer to Fig. 2, the op amp has open-loop gain (A) of 10^3 , the 3dB bandwidth (f_H) of 100 Hz and output resistance $R_o = 10^5 \Omega$. Find the voltage gain (V_o/V_i), 3dB bandwidth (f_{HF}) and output resistance (R_{of}) of the closed-loop circuit.
3. (10%) For the circuit in Fig. 3, neglect base currents and derive I_3/I_1 in term of I_{S1}, I_{S2}, I_{S3} and I_{S4} , where I_{Si} is the saturation current corresponding to the BJT Q_i .

 


Fig. 1

 


Fig. 2

 


Fig. 3

4. (17%) The small-signal equivalent circuit of a two-stage amplifier is shown in Fig.4, where $R_{in} = 1 \text{ M}\Omega$, $C_c = 1 \mu\text{F}$, $g_{m1} = 100 \mu\text{A}/\text{V}^2$, $g_{m2} = 125 \mu\text{A}/\text{V}^2$, $R_1 = 200 \text{ k}\Omega$, $R_2 = 250 \text{ k}\Omega$, $C_1 = 0.5 \text{ pF}$ and $C_2 = 2.5 \text{ pF}$.
 - (a) Determine the midband gain (in dB).
 - (b) If a compensation capacitor (2pF) is added between nodes 1 and 2, estimate the dominant pole frequency (in Hz).
 - (c) Roughly sketch the magnitude response of the amplifier gain (v_o/v_{in}) after compensation, and indicate the -3dB frequencies (in Hz) in your plot.
 - (d) Find the zero results from the compensation capacitor. Is the zero located in the right-half or the left-half plane?

 


Fig. 4

大同大學 九十五 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 2/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

5. (17%) Consider the circuit shown in Fig. 5, where $R_G=1M\Omega$, $R_{sig}=200k\Omega$, $R_L=10k\Omega$, $V_{DD}=-V_{SS}=5V$, $m_n C_{ox}=100\mu A/V^2$, $(W/L)_1=(W/L)_2=20$ and $V_{tn}=0.6V$. Assume the coupling capacitors to be sufficiently large so as to act as short circuits at the signal frequencies of interest. Neglect the body effect.

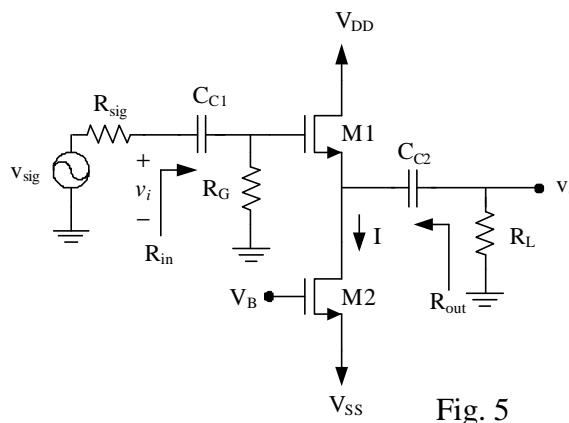


Fig. 5

- Transistor M2 is used as a current source to provide $I=1mA$. Find the value for V_B , and the minimum drain voltage for M2 to act as a current source.
- Find R_{out} and $A_v (v_o/v_i)$. ($\lambda=0.04 V^{-1}$)
- Find R_{in} , and the overall small-signal voltage gain $G_v (v_o/v_{sig})$.
- If the bodies of the two transistors are tied together, which transistor suffers from body effect?

6. (16%) The circuits of Fig. 6 show different implementations of an inverter whose output is connected to a capacitor. Assume $V_{tn}=0.4 V$ for $0.13 \mu m$ technology.

- Which one of the circuits consumes static power when the input is high? Why?
- Which one of the circuits consumes static power when the input is low? Why?
- V_{OH} of which circuit(s) is $1.2 V$? Why?
- V_{OL} of which circuit(s) is $0 V$? Why?
- V_{OH} or V_{OL} of which circuit(s) depends on the size of the devices? (i.e. which circuit(s) is(are) a ratio circuit(s)?)

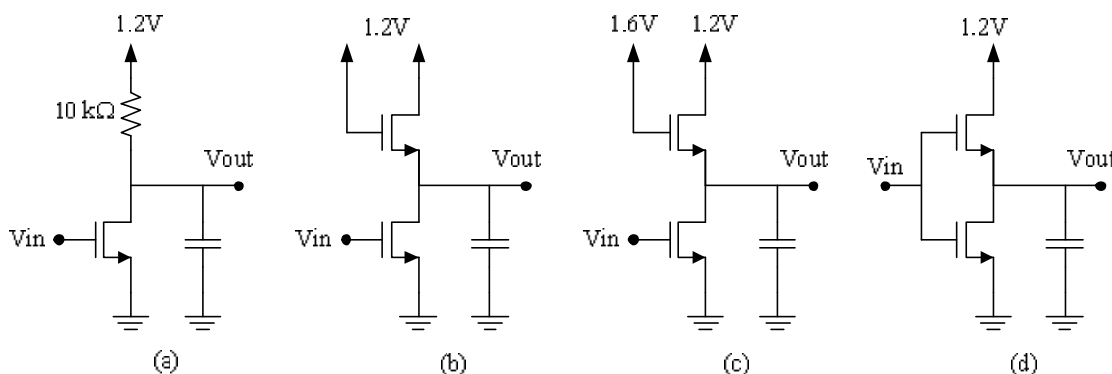


Fig. 6

7. (16%) Design a 5 GHz ring oscillator using CMOS inverters. Assume the specified inverter has the propagation delay of 0.02 ns with the power supply V_{DD} of 1.8 V, the input capacitor of 30 fF and the output capacitor of 50fF.

- How many stages of inverter in cascade do you use to form this ring oscillator?
- Neglect the short-circuit power dissipation, what is average power consumption of this ring oscillator design in part (a)?