

# 大同大學 96 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 1/1 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

- (16%) (a) The Widlar current source shown in Fig. 1 is biased at  $V^+ = 5V$ ,  $V^- = -5V$ ,  $V_{BE1} = 0.7V$  with resistor  $R_1 = 9.3 K\Omega$  and  $R_E = 9.58 K\Omega$ . Calculate  $I_{REF}$  and  $I_O$ .  
 (b) Derive the output resistance ( $R_O$ ) and calculate it with BJT's  $V_A = 80 V$  and  $\beta = 100$ .

 


Fig. 1

 


Fig. 2

- (17%) Refer to Fig. 2, where  $I_{REF} = 100\mu A$  and all transistors have  $W/L = 100\mu m / 1.6\mu m$ ,  $\mu_n C_{ox} = 90\mu A/V^2$ ,  $\mu_p C_{ox} = 30\mu A/V^2$ ,  $1/\lambda_n = V_{An} = 12.8V$ ,  $1/|\lambda_p| = |V_{Ap}| = 19.2V$ , and the body effect factor  $\chi = 0.15$  for Q1. Calculate  $g_{m1}$ ,  $g_{mb1}$ ,  $r_{o1}$ ,  $r_{o2}$ , the voltage gain  $A_v = \frac{v_o}{v_i}$  and the input resistance  $R_{in}$ .
- (10%) (a) Design an inverting opamp circuit for which the gain is  $-5V/V$  and an input resistance of  $10k\Omega$ . Draw the circuit.  
 (b) If the opamp has an open-loop gain of  $600V/V$ , determine the actual gain of the inverting opamp circuit designed in part (a).
- (24%) Consider the differential amplifier shown in Fig. 3, where  $(W/L)_1 = (W/L)_2 = 100$ ,  $(W/L)_{B1} = 20$ ,  $(W/L)_{B2} = 100$ , and  $\mu_n C_{ox} = 2.5 \times \mu_p C_{ox} = 100\mu A/V^2$ ,  $V_{tn} = -V_{tp} = 0.6V$ ,  $\lambda_n = \lambda_p = 0.04 V^{-1}$ . For DC bias calculations, neglect channel-length modulation effect.  
 (a) For  $I_{bias} = 40\mu A$ , find the required value of  $R$ .  
 (b) If the DC voltage at the output is  $2V$ , find the  $W/L$  ratio for M3 and M4.  
 (c) Determine the low-frequency differential gain ( $v_{out}/v_d$ ).  
 (d) Estimate the  $-3dB$  frequency in Hz.  
 (e) Find the input common-mode ( $V_{CM}$ ) range.
- (25%) (a) Draw the schematic diagram of a CMOS inverter with the substrate connection.  
 (b) Draw the input and output voltage transfer characteristic curve with  $V_{DD} = 3.3$  volts,  $V_{tn} = |V_{tp}| = 1$  volt, and define the range in which both transistors are saturated.  
 (c) Draw the input voltage  $V_{in}$  and the drain current  $I_{DN} = |I_{Dp}|$  transfer curve.  
 (d) Find the  $(W/L)_{NMOS}/(W/L)_{PMOS}$  if noise margin  $NM_0 = NM_1$  is required. Assume  $\mu_n C_{ox} = 115 \mu A/V^2$  and  $\mu_p C_{ox} = 30 \mu A/V^2$ . You must label the critical break points in the curves.
- (8%) The identical NMOS transistors are connected as Fig. 4. Determine the output voltage ( $V_o$ ) in terms of  $V_{DD}$  and  $V_t$ , where  $V_t$  is the threshold voltage of device. (Neglect the body effect).

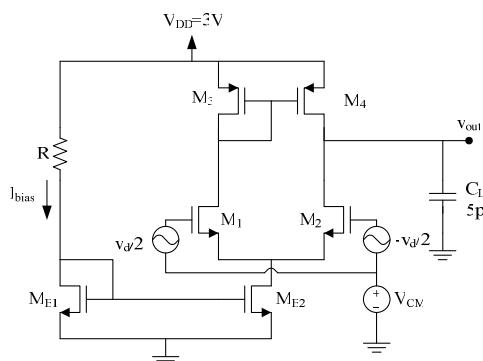


Fig. 3

 


Fig. 4