

# 大同大學 97 學年度研究所碩士班入學考試試題


考試科目：電力系統

所別：電機工程研究所

第 全 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

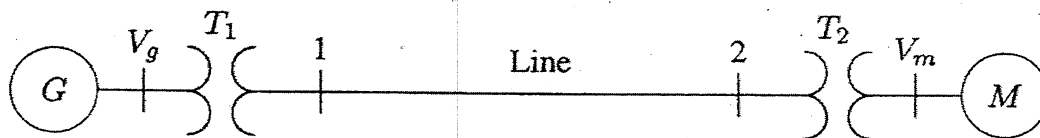1. An industrial dryer operates at 600 volt and requires 50A. The unit consists of a fan in parallel with a heater. The fan draws 20kW and has a lagging power factor 0.8. Use a power triangle to find the resistance of the heater, assuming that it has unity power factor. (25%)
  
2. A balanced wye-connected load is connected to a 60Hz three-phase source with  $V_{ab}=208\angle 0^\circ$  volt. The load has  $pf=0.5$  lagging, and each phase draw  $P_\phi=6kW$ . (a) Calculate line current  $I_l$  and find  $Z_y$ ,  $\underline{I}_a$ ,  $\underline{I}_b$ , and  $\underline{I}_c$  in polar form. (b) What value of capacitance C should be put in parallel with each load element to minimize the current from the source, and what is the resulting line current? (Assuming the source is positive sequence!) (25%)
  
3. The three-phase power and line-line ratings of the electric power system shown in the following figure.



$G_1$ :	60MVA	20 kV	$X=9\%$
$T_1$ :	50MVA	20/200 kV	$X=10\%$
$T_2$ :	50MVA	200/20 kV	$X=10\%$
M:	43.2MVA	18 kV	$X=8\%$
Line:		200 kV	$Z=120+j200\Omega$

- (a) Draw an impedance diagram showing all impedances in per-unit on a 100-MVA base. Choose 20 kV as the voltage base for generator.
- (b) The motor is drawing 45MVA, 0.80 power factor lagging at a line-to-line terminal voltage of 18 kV. Determine the terminal voltage of the generator in per-unit and in kV. (25%)
  
4. The zero-, positive-, and negative-sequence bus impedance matrices for a three-bus power system are
 
$$Z_{bus}^0 = j \begin{bmatrix} 0.20 & 0.05 & 0.12 \\ 0.05 & 0.10 & 0.08 \\ 0.12 & 0.08 & 0.30 \end{bmatrix} pu$$

$$Z_{bus}^1 = Z_{bus}^2 = j \begin{bmatrix} 0.16 & 0.10 & 0.15 \\ 0.10 & 0.20 & 0.12 \\ 0.15 & 0.12 & 0.25 \end{bmatrix} pu$$
 Determine the per unit fault current and the bus voltage at bus 1 during fault for a bolted double line-to-ground fault at bus 2. (25%)