

# 大同大學 98 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. The circuit as shown in Fig.1,  $R_1 = 5\text{ K}\Omega$ ,  $R_2 = 10\text{ K}\Omega$ , the diode cut-in voltage  $V_{D0} = 0.7\text{V}$ , draw the  $V_o$  vs  $V_i$  plot, calculate and indicate the voltages at the breakpoints. (13%)

 


Fig.1

 


Fig.2

2. Three-stage amplifier as shown in Fig.2, neglect other capacitances and assuming identical MOS transistors with  $\lambda=0$ .

(a) In terms of transconductance  $g_m$ ,  $R_D$  and  $C$ , derive the transfer function  $A(s) = \frac{V_o}{V_i}$ . (7%)

(b)  $A(j\omega) = A(s)|_{s=j\omega} = |A(j\omega)|e^{j\phi}$ , write an expression for  $|A(j\omega)|$ , and draw the Bode plot  $|A(j\omega)|_{dB}$  vs  $\omega$  (log scale). (6%)

(c) If we apply negative feedback with feedback factor  $\beta=1$  around the amplifier, determine the condition for the amplifier to be stable. (6%)

3. For the MOS current-steering circuit shown in Fig. 3,  $I_{REF}=100\ \mu\text{A}$ ,  $\mu_n C_{ox} = 160\ \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 64\ \mu\text{A}/\text{V}^2$ ,  $V_{tn}=0.5\text{V}$ ,  $V_{tp}=-0.6\text{V}$ ,  $(W/L)_1=20$ ,  $(W/L)_2=30$ ,  $(W/L)_{3,4}=75$  and  $(W/L)_{5,6}=150$ .

(a) Neglecting channel-length modulation and body effects, determine  $I_1$ ,  $I_2$  and  $V_{G3}$ . (8%)

(b) Determine the maximum allowable voltage at the output. (4%)

(c) Find the output resistance  $R_o$ . ( $\lambda = 0.05\ \text{V}^{-1}$ ) (5%)

4. Consider the differential pair shown in Fig.4, where  $\mu_n C_{ox} = 160\ \mu\text{A}/\text{V}^2$ ,  $V_{tn}=0.5\text{V}$  and  $(W/L)_{1,2}=20$ .

(a) Find the minimum required voltage for  $v_{IN}$  such that  $i_{D1} = I_B$  and  $i_{D2} = 0$ . (4%)

(b) Draw  $i_{D1}$  and  $i_{D2}$  with respect to  $v_{IN}$  for Fig.4. Show the critical voltage and current values. (5%)

 


Fig.3

 


Fig.4

<背面繼續>

# 大同大學 98 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 2/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

〈接前頁〉

5. Consider the common-source amplifier shown in Fig.5, where  $V_{DD}=3V$ ,  $\mu_n C_{ox} = 160 \mu A/V^2$ ,  $\mu_p C_{ox} = 64 \mu A/V^2$ ,  $V_{tn}=0.5V$ ,  $V_{tp}=-0.6V$ ,  $(W/L)_1=20$ ,  $(W/L)_{2,3}=50$  and  $I_B=100 \mu A$ . The DC voltage  $V_{IN}$  is chosen such that all transistors are biased in the saturation region.

 


Fig.5

(a) Estimate the low-frequency voltage gain for the amplifier. ( $\lambda_n = \lambda_p = 0.05 V^{-1}$ ) (5%)

(b) Estimate the -3dB bandwidths for the amplifier with  $R_S = 1M\Omega$  and  $C_L = 5pF$ .

Assume  $C_L$  is the total capacitance at the output node. ( $C_{gs1}=0.2pF$  and  $C_{gd1}=0.02pF$ ) (5%)

6. The circuits of Fig.6 show different implementations of an inverter whose output is connected to a capacitors. (20%)

(a) Which one of the circuits consumes static power when the input is high?

(b) Which one of the circuits consumes static power when the input is low?

(c)  $V_{OH}$  of which circuit(s) is 1.2 V?

(d)  $V_{OL}$  of which circuit(s) is 0 V?

(e) The proper functionality of which circuit(s) depends on the size of the devices?

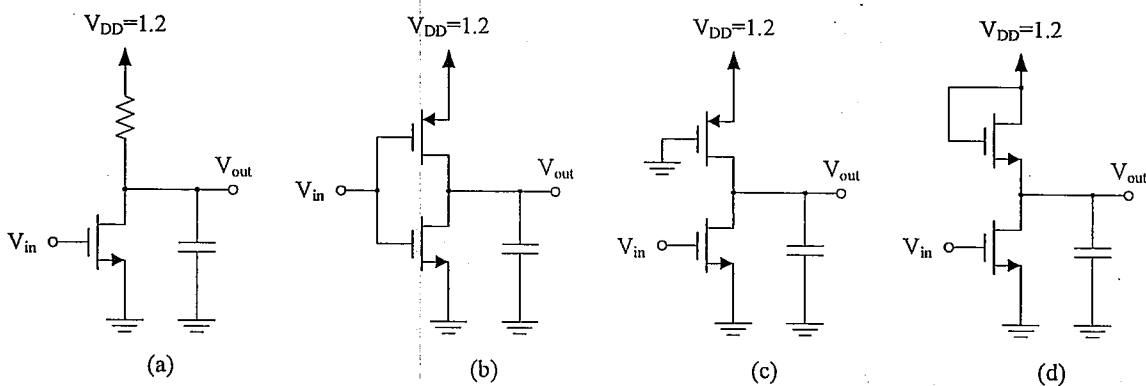


Fig.6

7. (a) Design a static CMOS gate that performs the Boolean function  $F = (A \oplus B)C + BC$ . You can use inverters to generate any complementary inputs needed. Sizing is not required here. (6%)

(b) Find the logic function for the circuit in Fig.7. (6%)

 


Fig.7