

大同大學 99 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

1. (10%) Assume the diodes in the circuit of Fig. 1 to be ideal.
 - (a) Derive the relationship of v_o and v_i .
 - (b) For $-10V \leq v_i \leq 10V$, draw the v_o vs v_i plot and indicate the voltages at the breakpoints.

 


Fig. 1

 


Fig. 2

2. (24%) The MOSFETs in the circuit of Fig. 2 are matched, having $\mu_n C_{ox} (W/L)_n = \mu_p C_{ox} (W/L)_p = 1 \text{ mA/V}^2$, $|V_{tn}| = |V_{tp}| = 0.5 \text{ V}$, and the resistance $R = 1 \text{ M}\Omega$.
 - (a) For G and D open, calculate the dc voltage at G (V_G) and dc drain current $I_{D1}(Q1)$ and $I_{D2}(Q2)$.
 - (b) For finite r_o ($\lambda_n = |\lambda_p| = 0.05 \text{ V}^{-1}$), draw the small-signal equivalent circuit, calculate the voltage gain (v_d / v_g) from G to D and find the input resistance (R_{in}) at G.
3. (10%) Find V_1 , V_2 and $I_1 \sim I_3$ in the circuit shown in Fig. 3. Assume $|V_{BE}| = 0.7 \text{ V}$ and $\beta = \infty$.

 


Fig. 3

 


Fig. 4

4. (14%) Consider the circuit shown in Fig. 4.
 - (a) Identify the feedback topology, and find the feedback factor β .
 - (b) If the opamp is ideal, find the closed-loop gain v_o/v_i .
 - (c) If the opamp gain is $A = 300$, find the closed-loop gain v_o/v_i .
 - (d) The ideal opamp is specified to have output current limits of $\pm 20 \text{ mA}$. If the circuit is fed with a low-frequency sine-wave signal of peak voltage 0.5 V , what is the lowest value of R_L for which an undistorted sine-wave output is obtained?

<背面繼續>

大同大學 99 學年度研究所碩士班入學考試試題

考試科目：電子學

所別：電機工程研究所

第 2/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 可以使用計算器。

〈接前頁〉

5. (12%) Consider the common-source amplifier shown in Fig.5, where $V_{DD}=3.3V$, $\mu_n C_{ox} = 200 \mu A/V^2$, $\mu_p C_{ox} = 80 \mu A/V^2$, $V_{tn}=0.5V$, $V_{tp}=-0.6V$, $(W/L)_1=20$, $(W/L)_{2,3}=50$ and $I_B=125 \mu A$.
- Calculate the required input DC voltage V_{IN} such that all transistors are biased in the saturation region.
 - Estimate the low-frequency voltage gain for the amplifier. ($\lambda_n = |\lambda_p| = 0.05 V^{-1}$)
 - Estimate the -3dB bandwidths for the amplifier with $C_L=5pF$. Assume C_L is the total capacitance at the output node.

 


Fig. 5

6. (18%)
- Draw the schematic diagram of a CMOS inverter with the substrate connection.
 - Find the input range which causes a direct-path current, i. e. both transistors are conducted simultaneously, if the inverter has the power supply $V_{DD} = 3.3$ Volts and the device threshold voltage is $V_{tn}=|V_{tp}| = 0.7$ volts.
 - If a CMOS inverter has the load capacitance C_L , then the direct-path current is function of the rise time, falling time and C_L . How does it affect the direct-path current when the rise time and C_L are increased respectively?
7. (12%) Please write down the Boolean functions of the CMOS circuits shown in Fig. 6 and identify these logic functions (AND, OR, XOR, MUX etc.) performed.

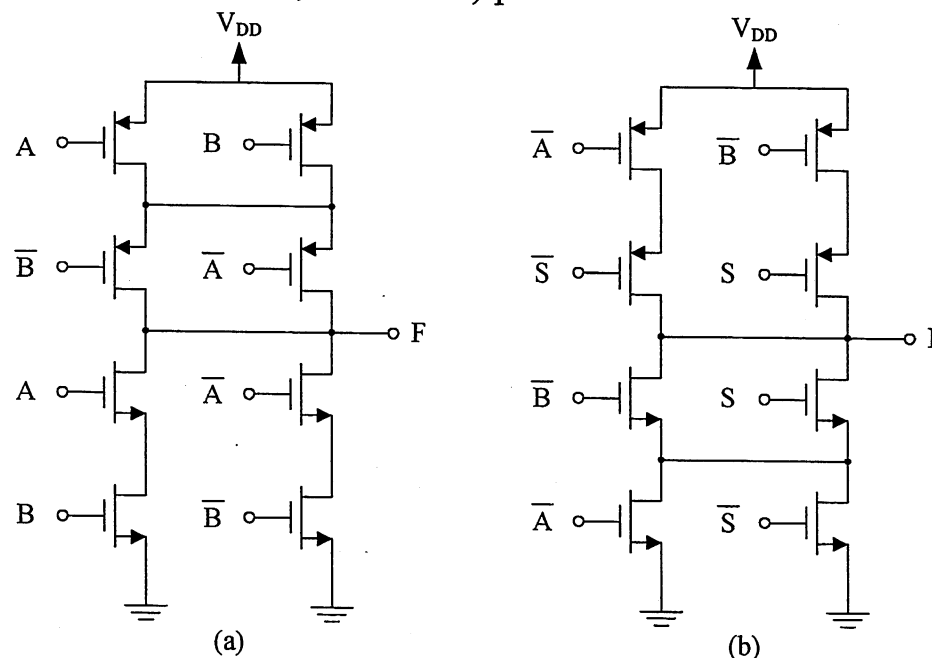


Fig. 6