

大同大學 103 學年度研究所碩士班入學考試試題

考試科目：計算機概論

所別：資訊工程研究所

第 1/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 不可以使用計算器。

Part I (資料結構)

- (5 points) What are the advantages of **height-balanced** binary trees over **normal** binary search trees?
- (10 points) Write the worst case running time (in **big-O** notation, i.e., $O(1)$, $O(\log n)$, $O(n)$, $O(n \log n)$, $O(n^2)$, etc.) for each of the following operations:
 - searching an **unordered list** with n items;
 - searching an **ordered list** with n items;
 - searching a **binary search tree** with n nodes;
 - searching a **height-balanced binary search tree** with n nodes;
 - searching a **hash table** with n keys.
- (15 points) Draw the following trees with **minimum height** that contains the 10 numbers from 1 to 10.
 - A **complete binary search tree**;
 - An **AVL tree** that is not complete;
 - A **2-3 tree**.
- (5 points) Let array A be $\{3, 9, 4, 7, 1, 6, 2, 8, 5\}$. What will A be after $f1(A, 0, 8)$ returns?
- (5 points) Let array A be $\{3, 9, 4, 7, 1, 6, 2, 8, 5\}$. What will A be after $f2(A, 0, 8)$ returns?

```
void f1(int a[], int p, int r)
```

```
{
    int i, j, t, x;
    x = a[r]; i = p - 1;
    for (j = p; j < r; j++)
        if (a[j] <= x) {
            i++; t = a[i]; a[i] = a[j]; a[j] = t;
        }
    t = a[i]; a[i] = a[r]; a[r] = t;
}
```

```
void f2(int a[], int p, int r)
```

```
{
    int t;
    if (p >= r) return;
    if (a[p] > a[r]) {
        t = a[p]; a[p] = a[r]; a[r] = t;
        f2(a, p+1, r);
    }
    else f2(a, p, r-1);
}
```

- (10 points) Write a C program, `rotateRight(int A[], int n)`, that can rotate an array of size n right by one element. For example, rotating $\{1, 2, 3, 4, 5\}$ will result in $\{5, 1, 2, 3, 4\}$.

Part II (基礎邏輯設計)

- Given the Boolean function $F(X, Y, Z) = \bar{X} + X(X + \bar{Y})(Y + \bar{Z})$
 - (5 points) Write out the **truth table** of the Boolean function.
 - (5 points) Draw the **logic diagram** of the Boolean function by using AND gates, OR gates, and NOT gates. The diagram should correspond exactly to the equation. Assume that the complements of the inputs are not available.
- (10 points) Given the Boolean function $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 7, 10, 11, 15)$, find the **minimal sum-of-products** expression of the function by using **Karnaugh map**.

大同大學 103 學年度研究所碩士班入學考試試題


考試科目：計算機概論

所別：資訊工程研究所

第 2/2 頁

註：本次考試 不可以參考自己的書籍及筆記； 不可以使用字典； 不可以使用計算器。

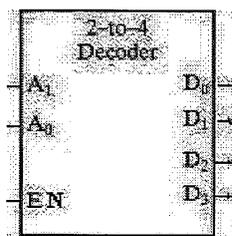9. (10 points) A **n-to- 2^n -line decoder with enable control** has **n** inputs, **2^n** outputs, and an enable control **EN**. When **EN = 0**, the operation of the decoder is disabled by setting all the outputs of the decoder to 0. When **EN = 1**, the operation of the decoder is enabled. Please design a **3-to-8-line decoder with enable control** by using **three 2-to-4-line decoders with enable control**. In your answer, please draw out the **block diagram** of the 3-to-8-line decoder by using the following schematic diagram representing the 2-to-4-line decoders with enable control.



10. A sequential circuit has two flip-flops A and B, one input X and one output Y. The state table of the circuit is given below.

Present State		Input X	Next State		Output Y
A	B		A	B	
0	0	0	0	1	1
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	1	1	0
1	1	1	1	1	0

Design the circuit with **D-type** flip flops. In your answer,

- (a) (6 points) derive the output function and the input equations of each flip flops;
 (b) (4 points) draw the logic diagram of the circuit.
11. (10 points) A **3-bit shift register** is to be operated according to the following function table using a control selection input S.

S	Register Operation
0	Left shift one bit
1	Right shift one bit

Design the shift register by using **D-type** flip flops. Please draw out the logic diagram of your design.

<<以下空白>>